

# **NOT, NOR & NAND Gates**

**Presented By:**

**Suraj Prakash**

**Asst. Professor**


# Outline

## ➤ **NOT, NOR & NAND Gate**

- Symbol
- Truth Table
- About Gate IC

# NOT Gate

## Symbol


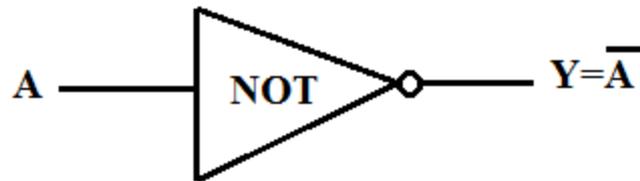


## Truth Table

Input	Output
A	$Y = \bar{A}$
0	1
1	0

- NOT gate has a single input and a single output.
- It is also known as an inverter, because it does the inversion of applied input.
- For the high (1) input it gives low (0) output and for low input it gives high output.

# NOT Gate IC and PIN Diagram

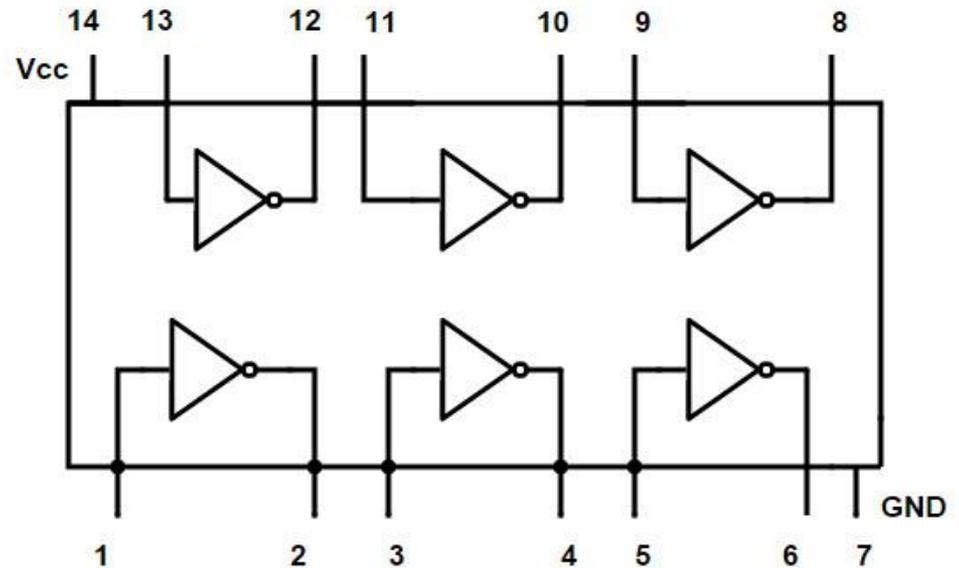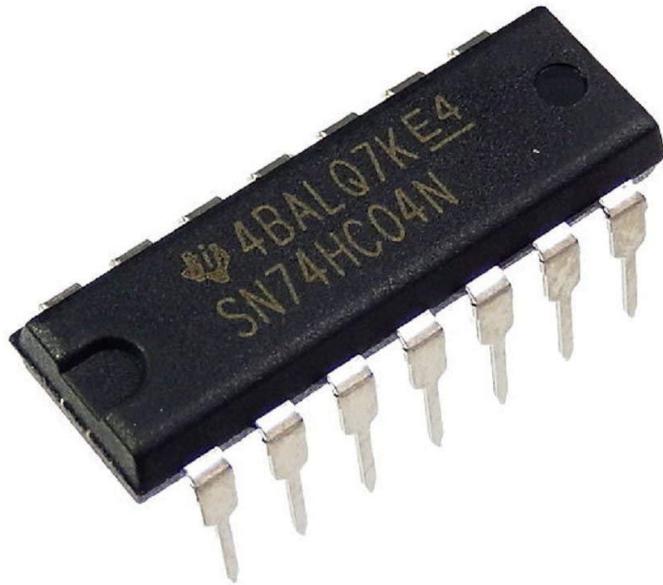


**IC 7404 NOT Gate IC**

**7404 IC PIN Diagram**

- IC 7404 is a NOT gate IC which contains six NOT gate as shown in PIN diagram. To activate the IC +Vcc is provided at PIN 14 and ground at PIN 7.

# NOR Gate

## Symbol

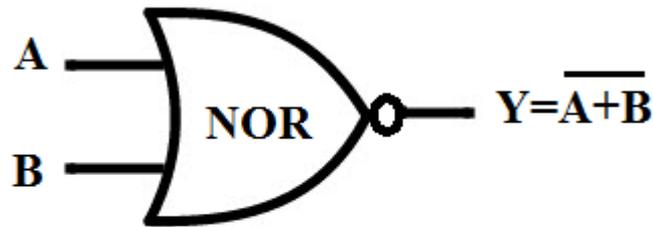


## Truth Table

Inputs		Output
A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

- It is a two input and one output terminal gate.
- The NOR gate is a cascade combination of OR – NOT gates.
- The output of NOR gate is high (1) when both the inputs are low (0) and the output is low when one or both inputs are high.

# NOR Gate IC and PIN Diagram

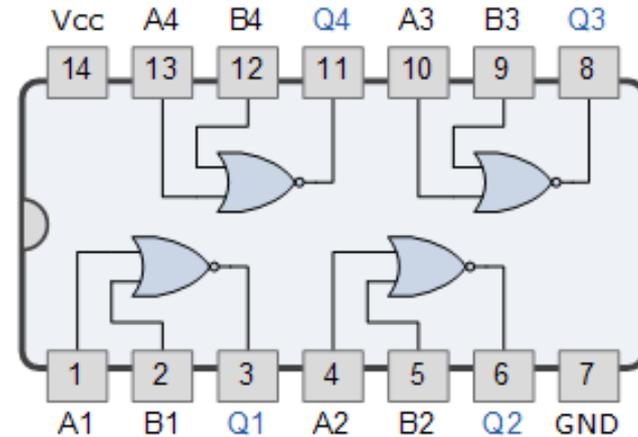

## IC 7402 NOR Gate IC

## 7402 IC PIN Diagram

- IC 7402 is a two input NOR gate IC which contains four NOR gate as shown in PIN diagram. To activate the IC +Vcc is provided at PIN 14 and ground at PIN 7.

# NAND Gate

## Symbol




## Truth Table

Inputs		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

- It is a two input and one output terminal gate.
- The NAND gate is a cascade combination of AND – NOT gates.
- The output of NAND gate is low (0) when both the inputs are high (1) and the output is high when one or both inputs are low.

# NAND Gate IC and PIN Diagram

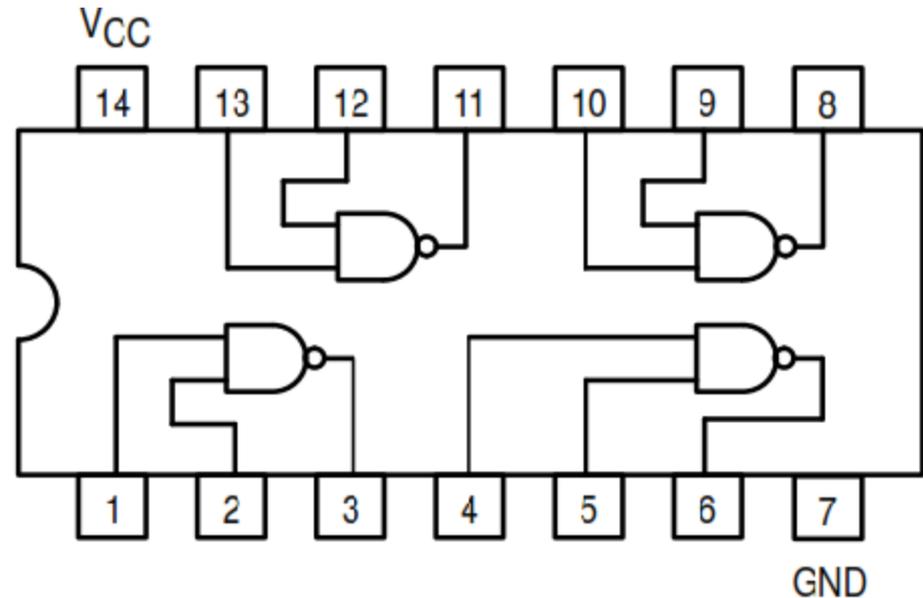

**IC 7400 NAND Gate IC**

**7400 IC PIN Diagram**

- IC 7400 is a two input NAND gate IC which contains four NAND gate as shown in PIN diagram. To activate the IC +Vcc is provided at PIN 14 and ground at PIN 7.